



MAKER JOURNAL

Name: _____

Date: _____

Project/Unit: Electrical Engineering

Lesson: 3

Write down important terms (vocabulary words) that appear in the video and write the meaning and/or draw a picture.

Vocabulary	Meaning
Example: Electron	Negatively-charged subatomic particle



MAKER JOURNAL

Name: _____

Date: _____

Draw pictures of your parallel and series circuits and record current and voltage measurements for each.

My Electrical Circuits

Make sure the multimeter is set to the appropriate amp and voltage settings before use.