

## *Breadboard Circuits*

Name: \_\_\_\_\_

Teacher: \_\_\_\_\_

Date: \_\_\_\_\_

Please circle ALL THE WORDS that describe the activity you just did:

Fun	Asking Questions	Boring
Creative	Like	Solving Problems
Dislike	Hard	I'm good at it
Easy	Thinking	Learning

Please answer the following questions as well as you can.

1. Which of the following is the part of a circuit that provides the power?

- |            |               |
|------------|---------------|
| A. Battery | C. Switch     |
| B. Wire    | D. Light bulb |

2. Which of the following is the part of a circuit that turns it on/off?

- |            |               |
|------------|---------------|
| A. Battery | C. Switch     |
| B. Wire    | D. Light bulb |

3. Which of the following are types of circuits?  
 (Circle all that apply)

- |             |           |
|-------------|-----------|
| A. Parallel | C. Series |
| B. Square   | D. Round  |