

## *Breadboard Circuits*

Name: \_\_\_\_\_

Teacher: \_\_\_\_\_

Date: \_\_\_\_\_

Please answer the following questions as well as you can.

1. Which of the following is the part of a circuit that provides the power?
  - A. Battery
  - B. Wire
  - C. Switch
  - D. Light bulb
  
2. Which of the following is the part of a circuit used to turn it on and off?
  - A. Battery
  - B. Wire
  - C. Switch
  - D. Light bulb
  
3. Which of the following are types of circuits?  
(Circle all that apply)
  - A. Parallel
  - B. Square
  - C. Series
  - D. Round